



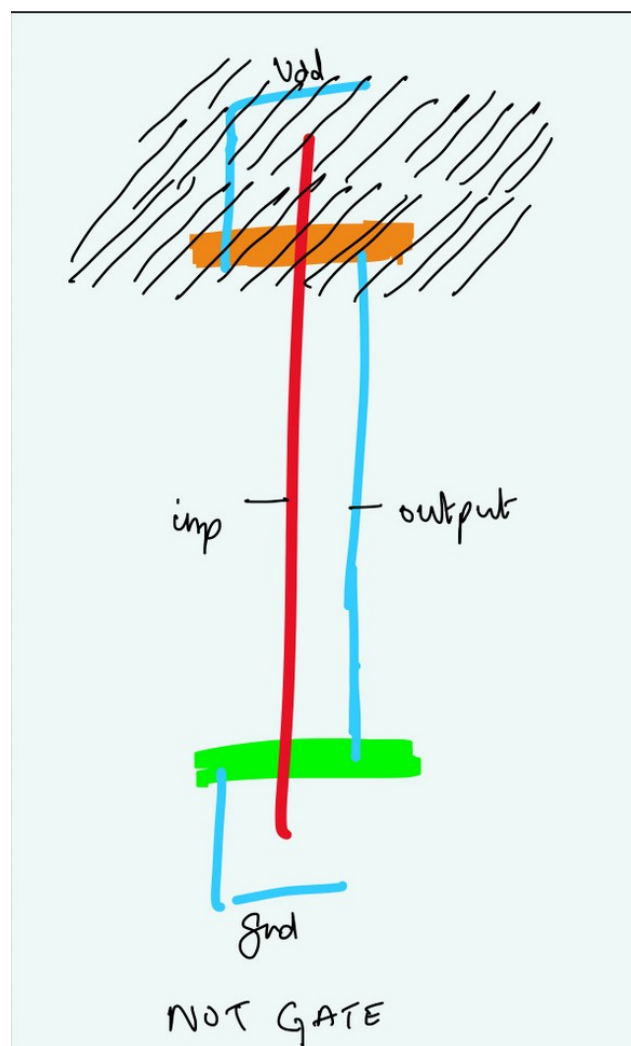


## GATES

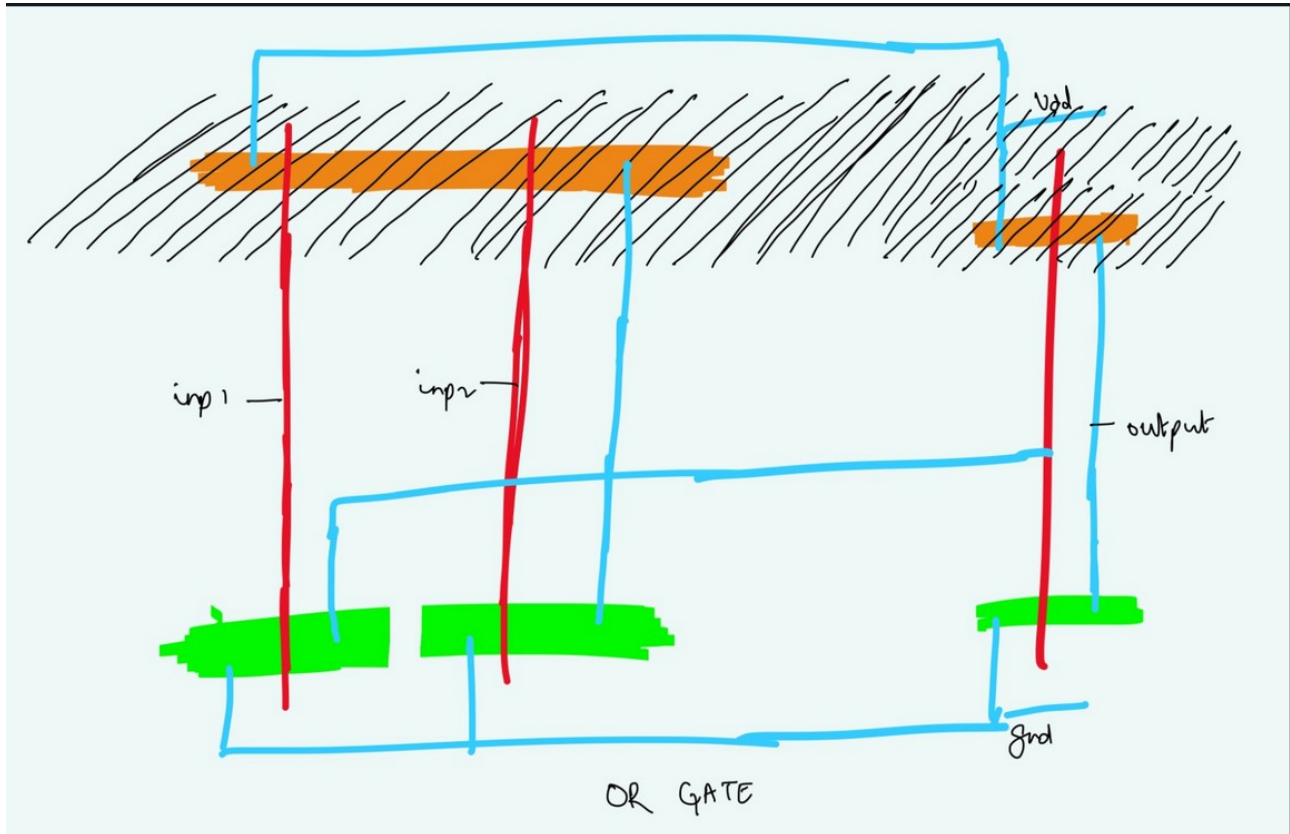


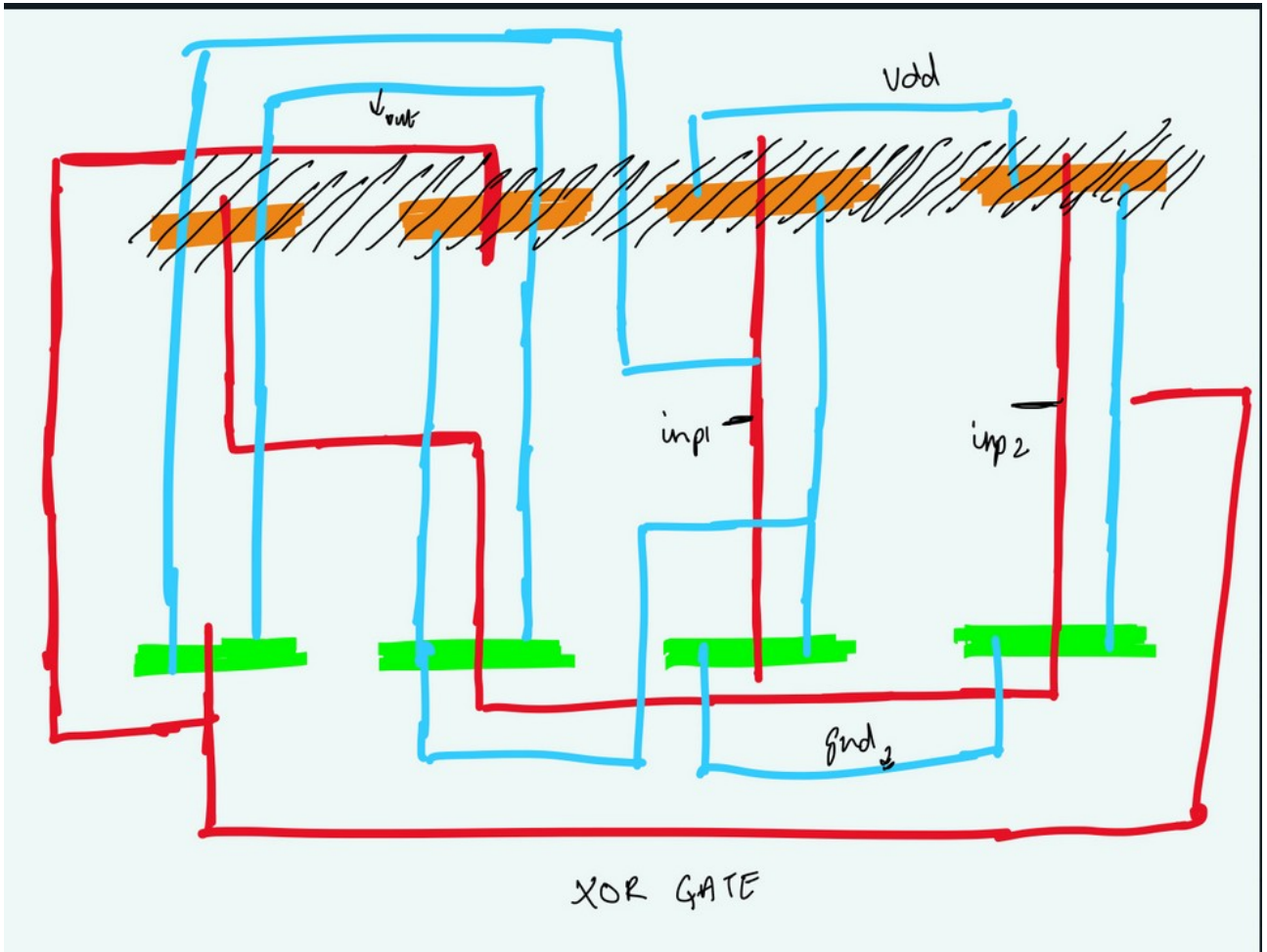

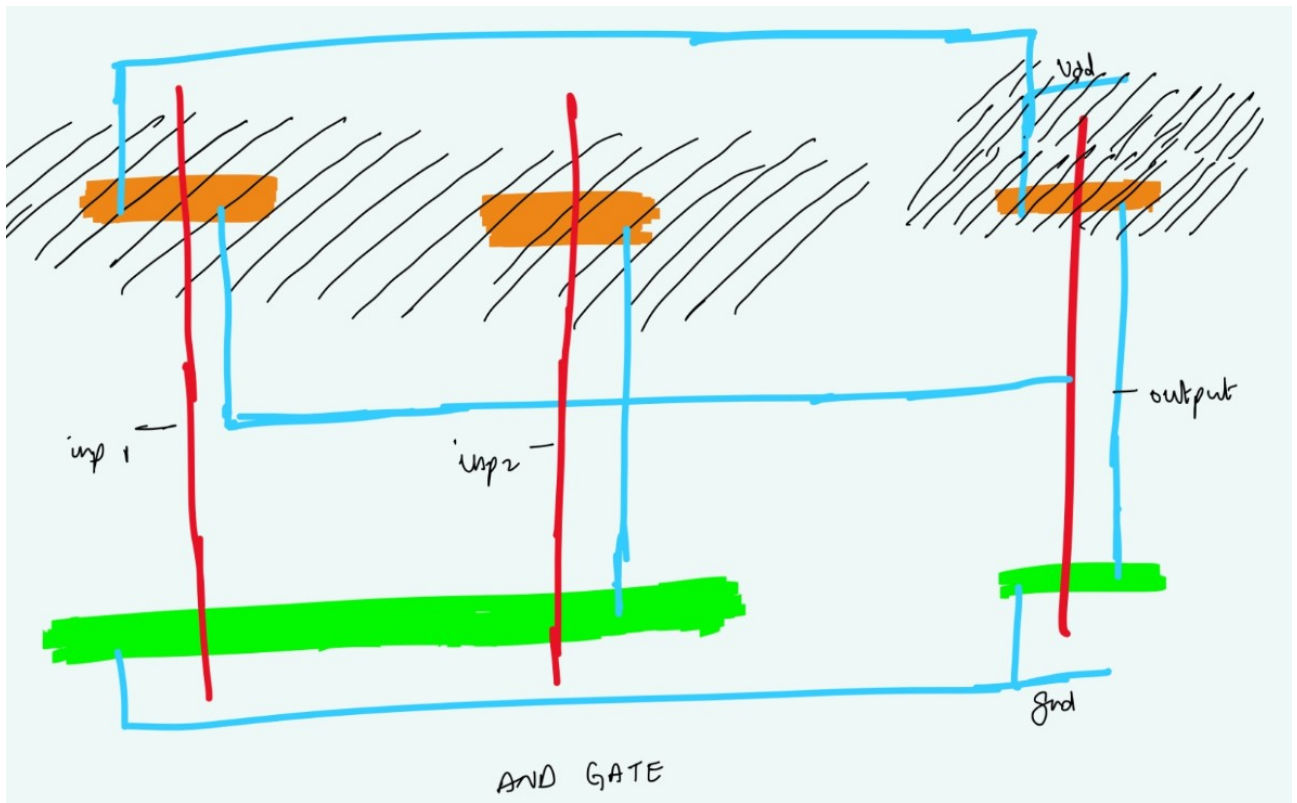


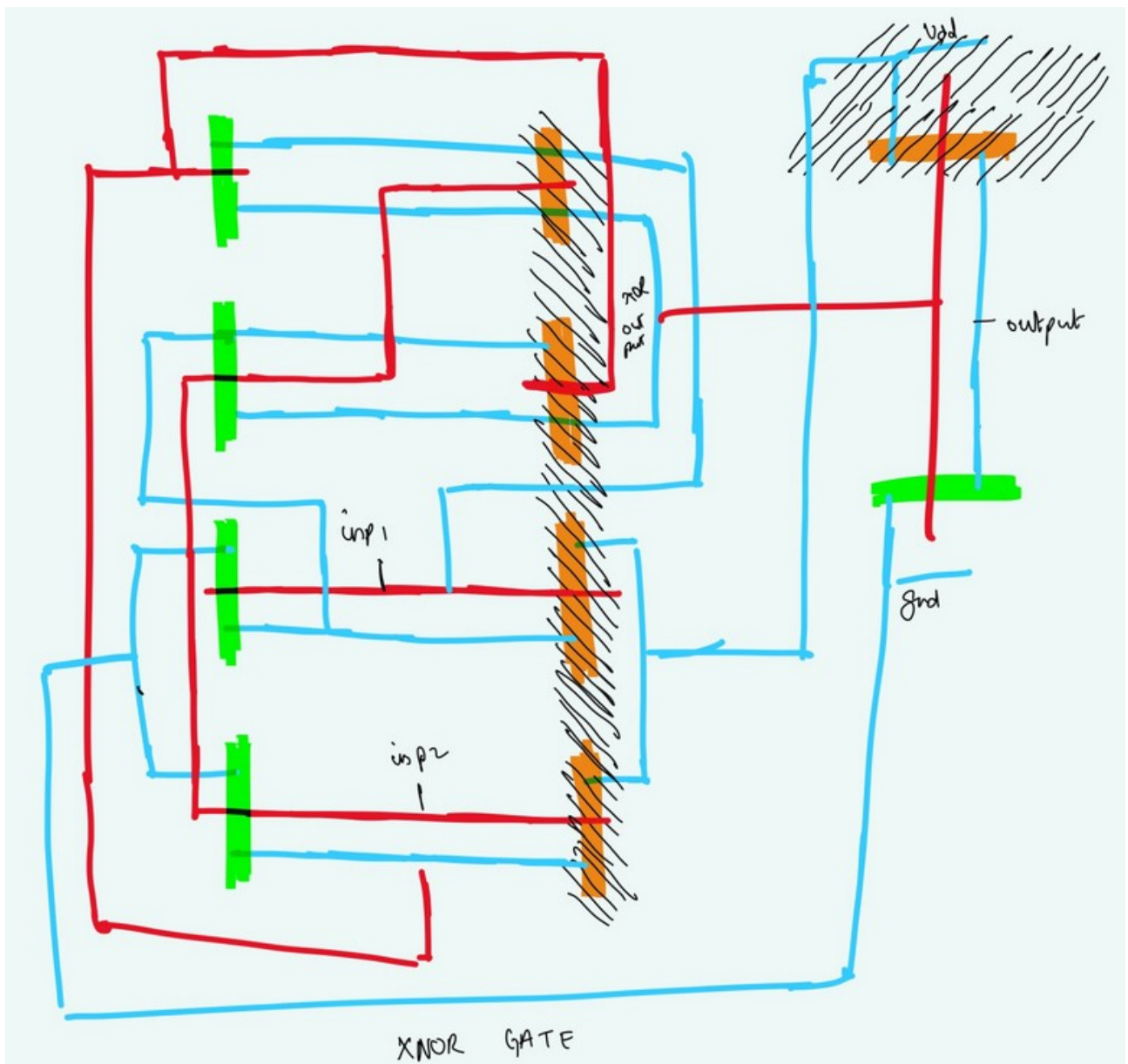


FULL ALU DESIGN


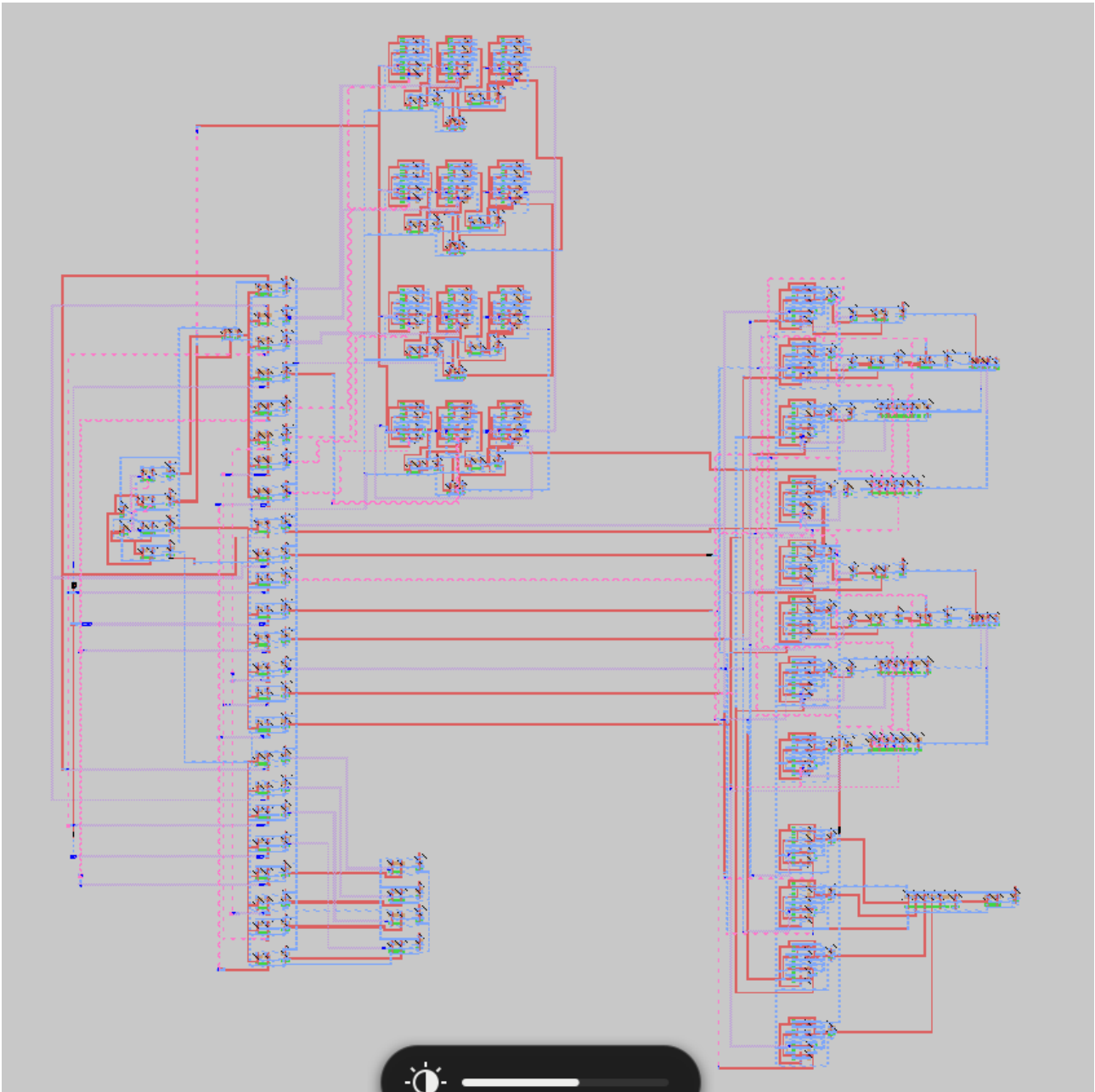


## GTK waveplot


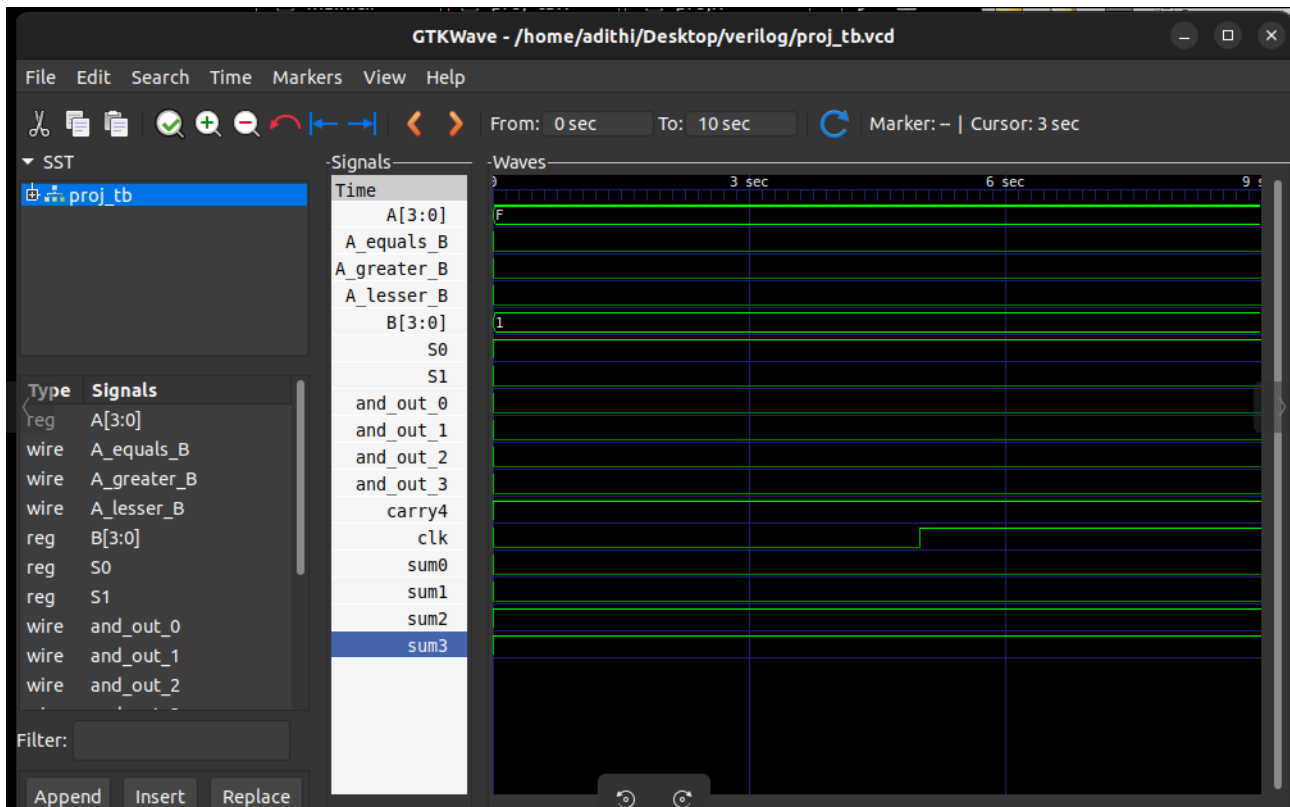


## ngspice plots

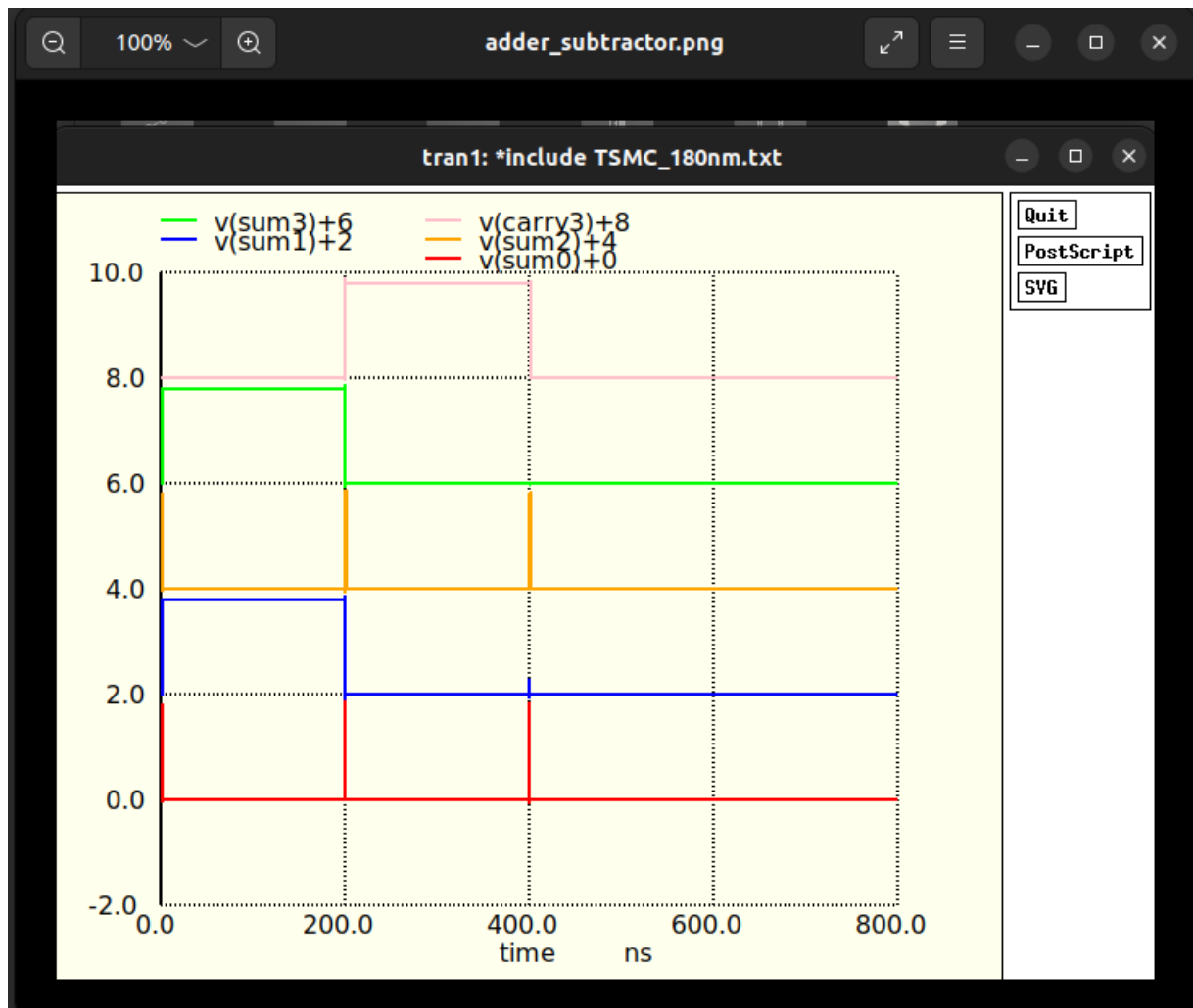


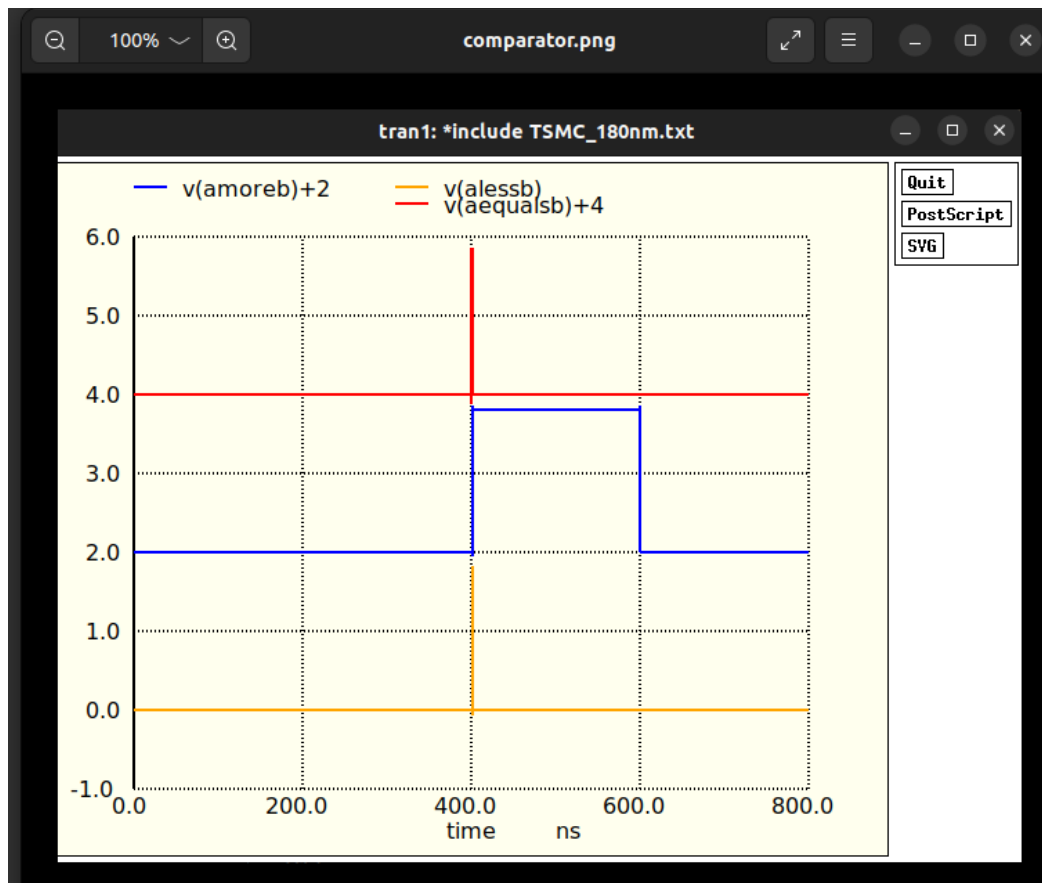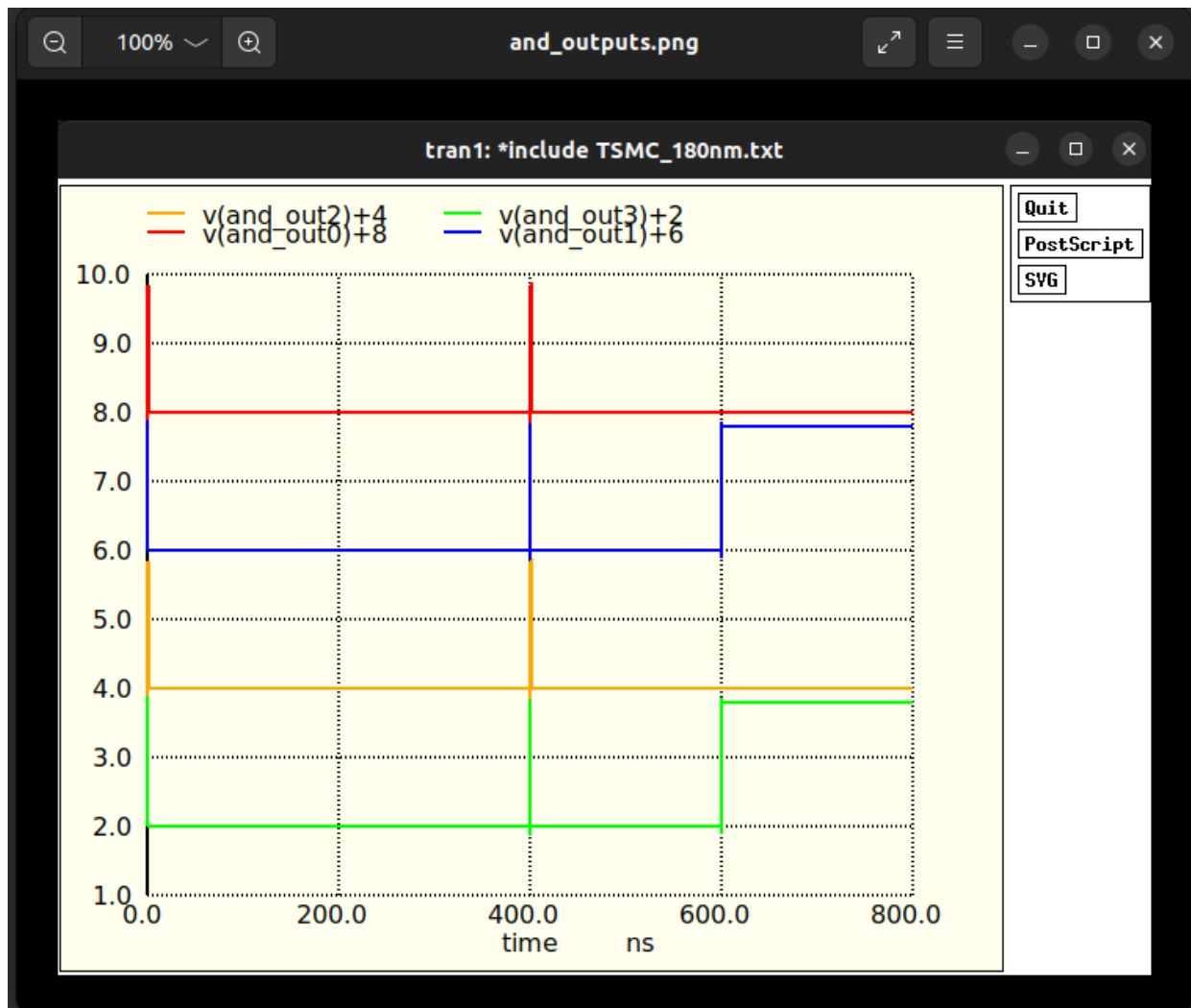




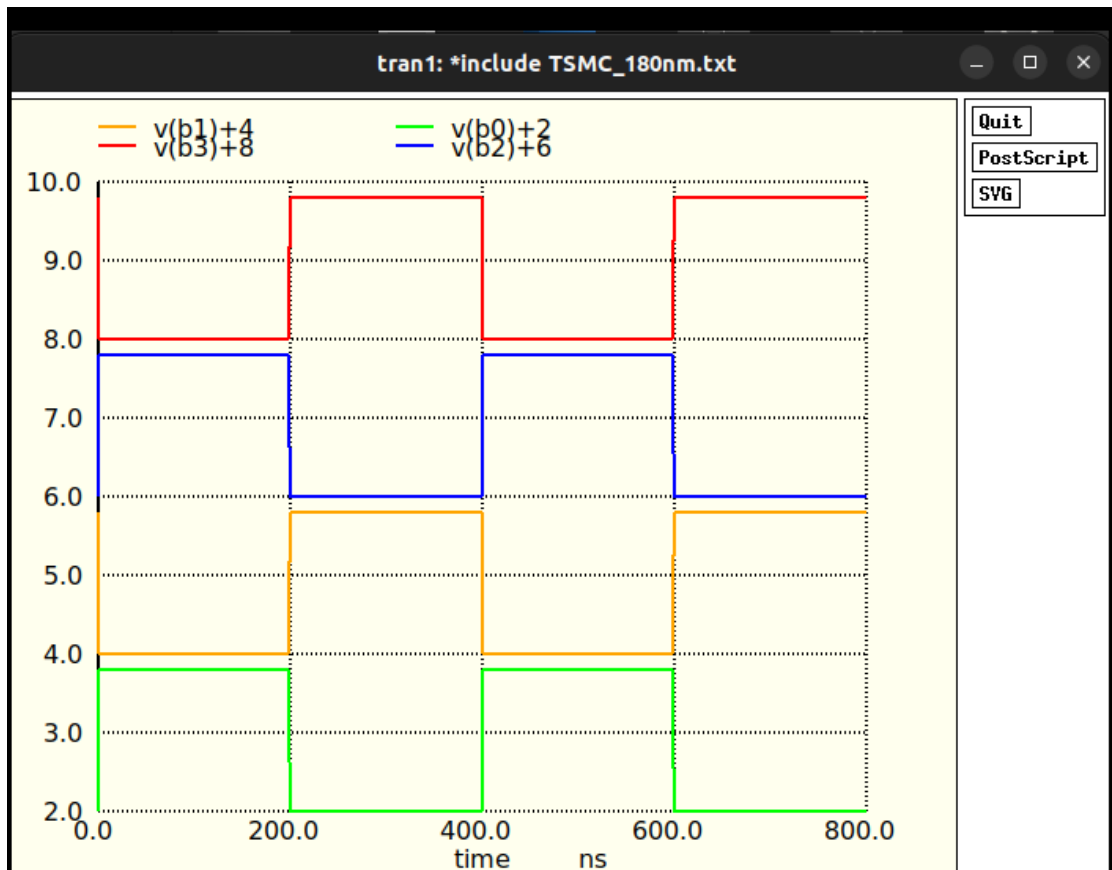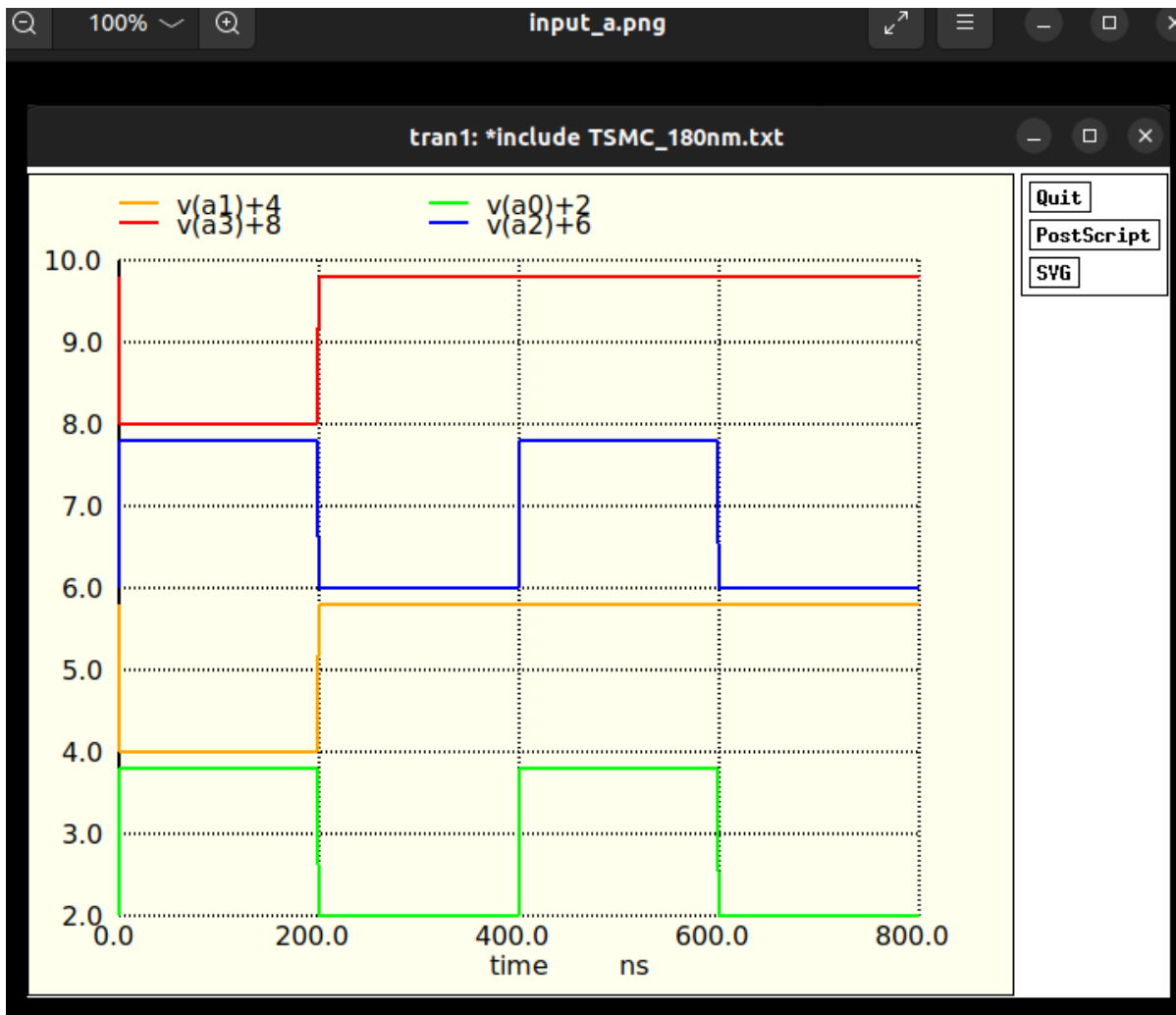




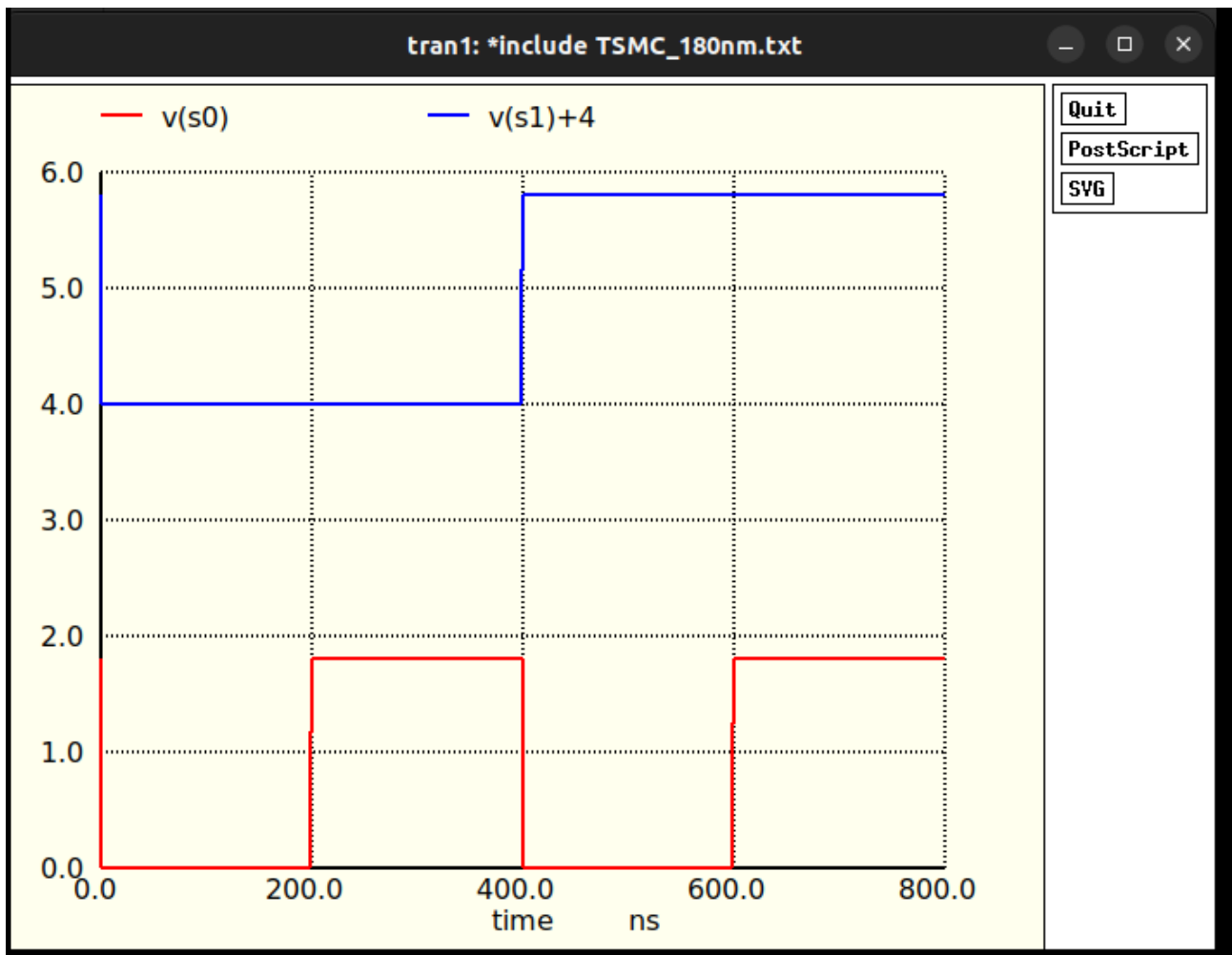




## PLOTS FROM MAGIC

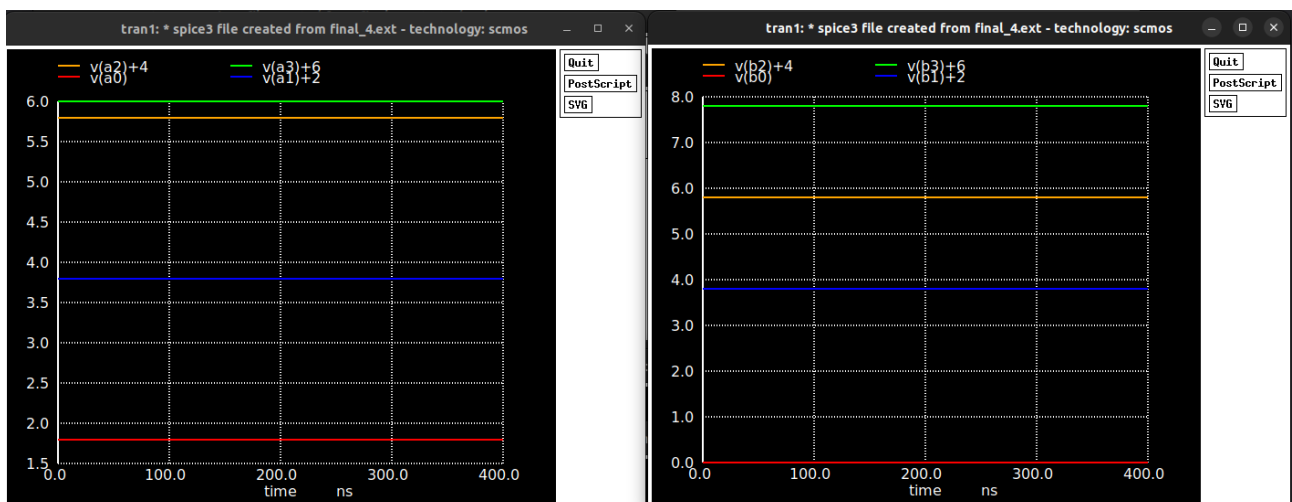

a – 0111


b - 1110

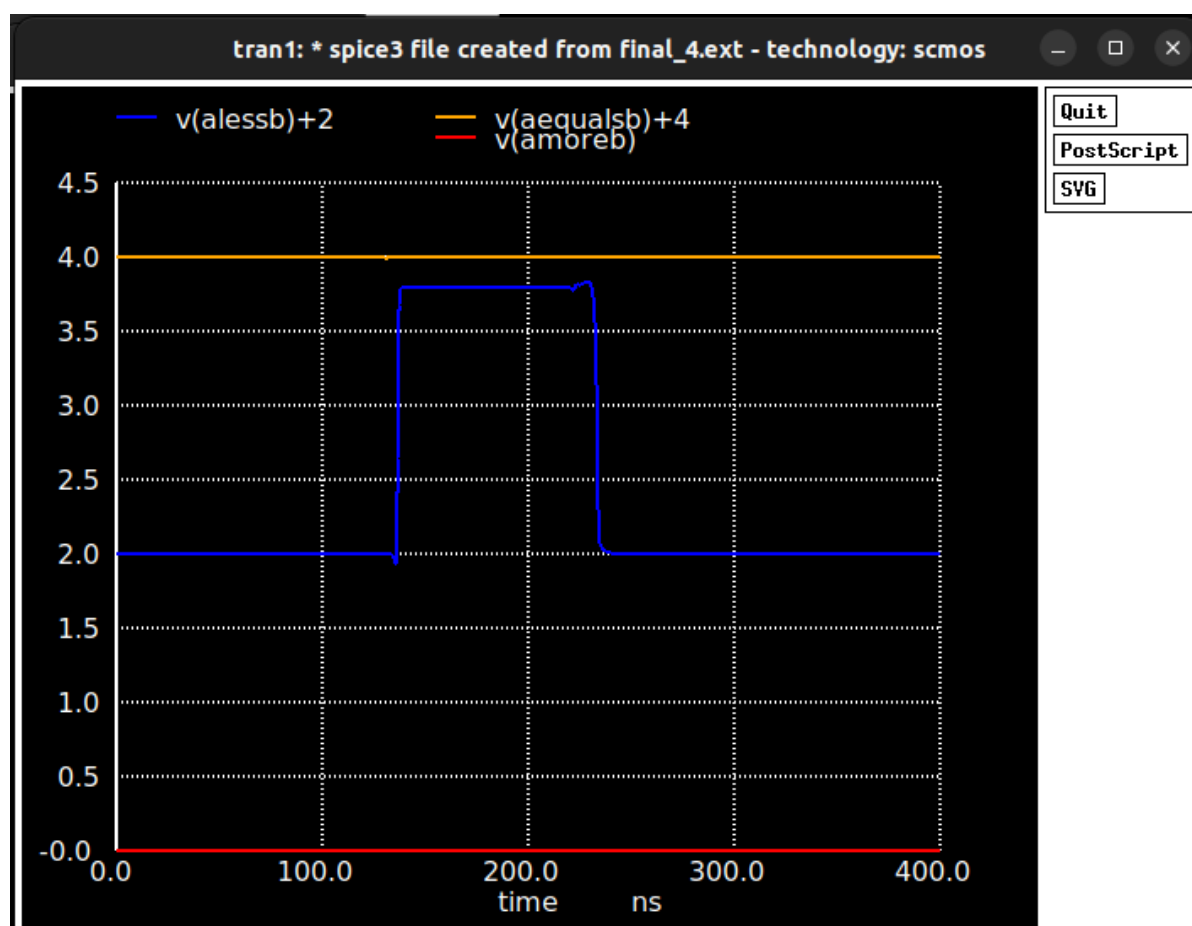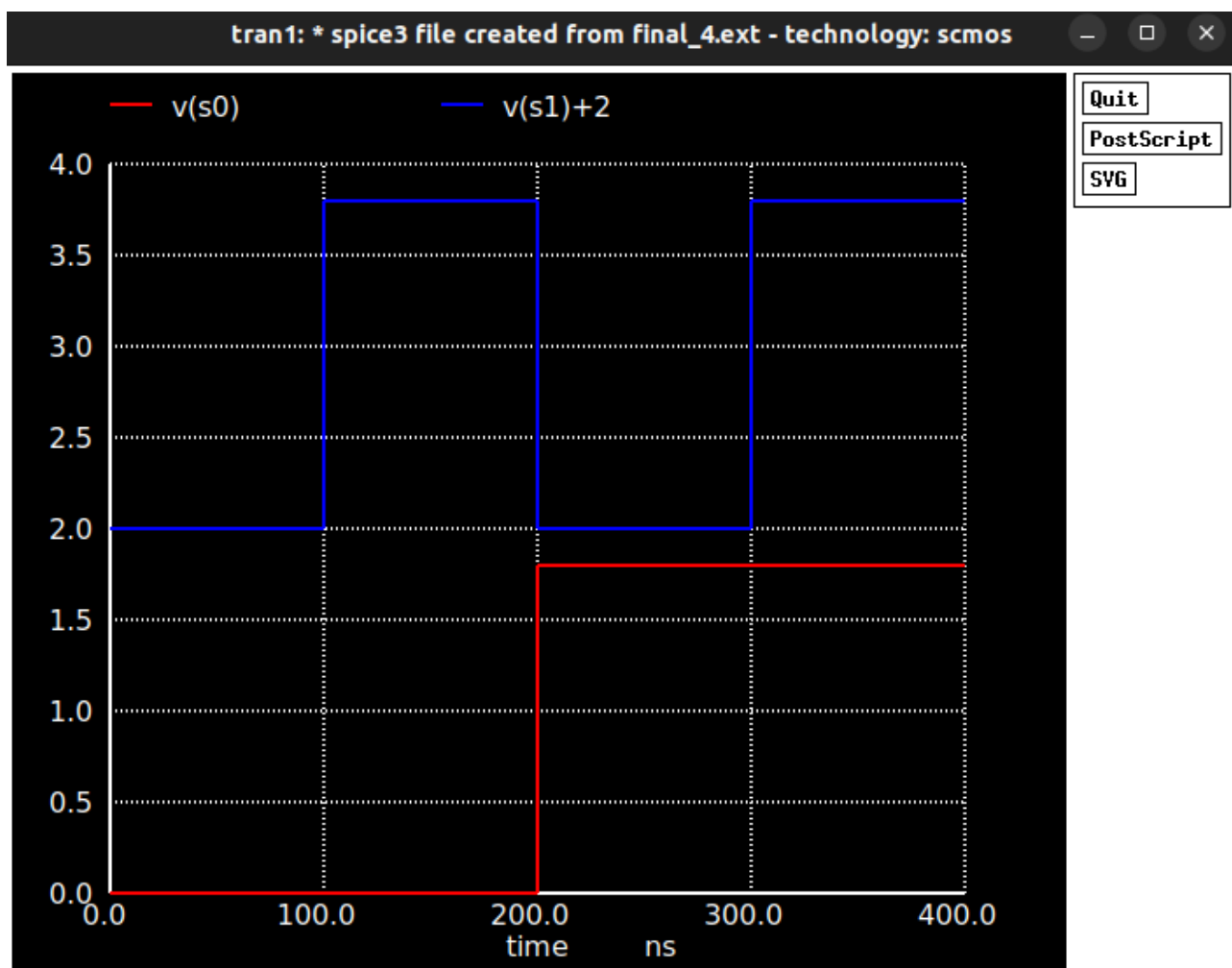

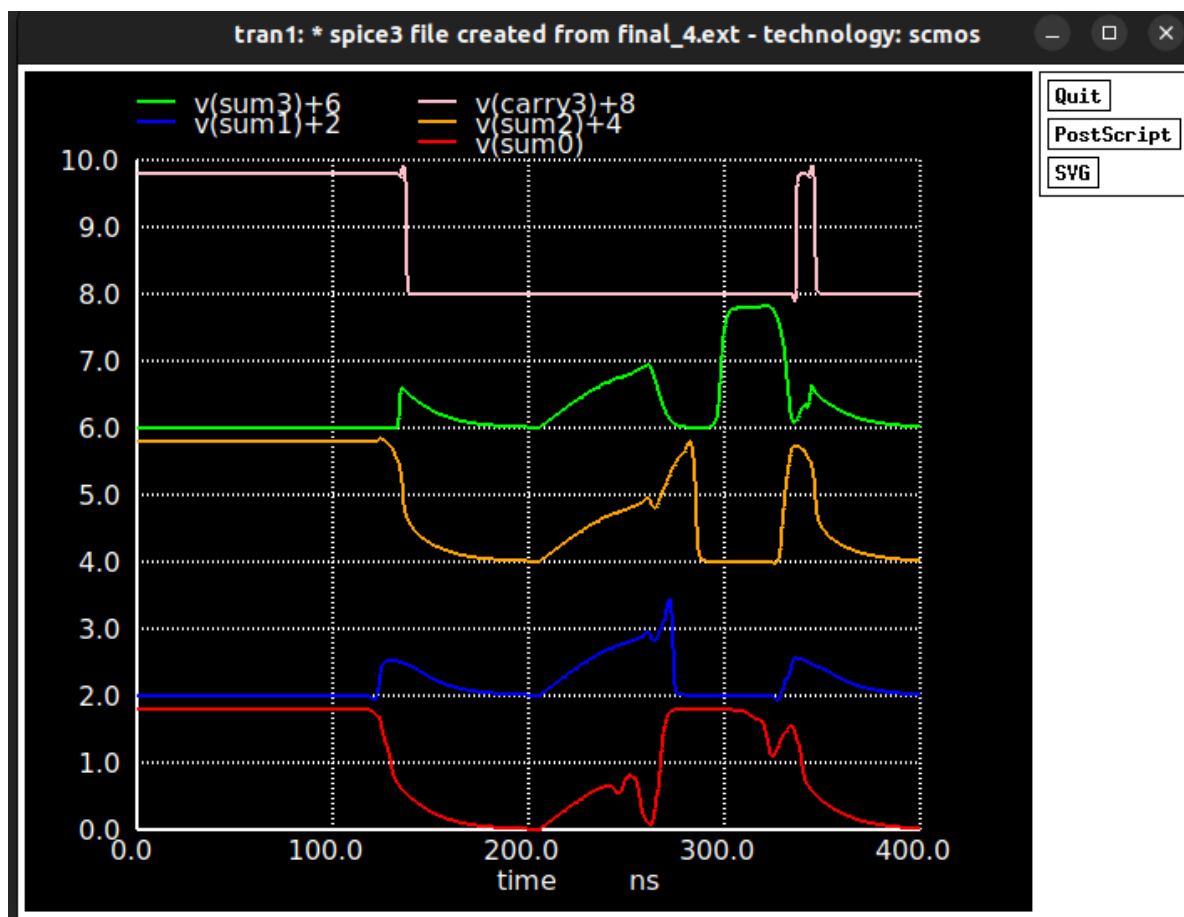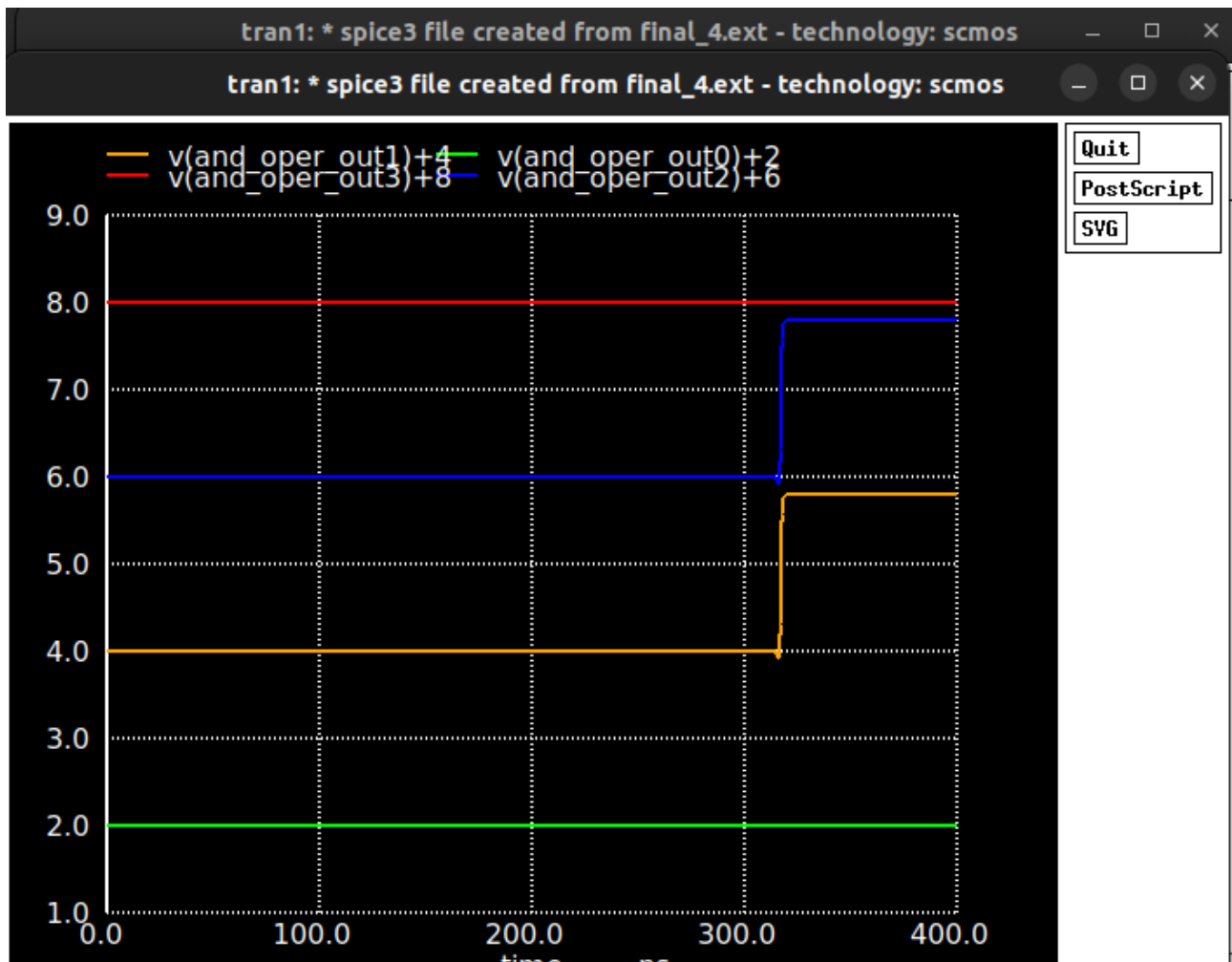


## DELAYS


adder delays

Delay Analysis >  adder_delay.txt					
1	tpd	=	1.28164e-08	input = A0	output = sum0
2	tpd	=	1.23021e-08	input = A0	output = sum1
3	tpd	=	1.29370e-08	input = A0	output = sum2
4	tpd	=	1.31226e-08	input = A0	output = sum3
5	tpd	=	1.28164e-08	input = A1	output = sum0
6	tpd	=	1.23021e-08	input = A1	output = sum1
7	tpd	=	1.29370e-08	input = A1	output = sum2
8	tpd	=	1.31226e-08	input = A1	output = sum3
9	tpd	=	1.28164e-08	input = A2	output = sum0
10	tpd	=	1.23021e-08	input = A2	output = sum1
11	tpd	=	1.29370e-08	input = A2	output = sum2
12	tpd	=	1.31226e-08	input = A2	output = sum3
13	tpd	=	1.28164e-08	input = A3	output = sum0
14	tpd	=	1.23021e-08	input = A3	output = sum1
15	tpd	=	1.29370e-08	input = A3	output = sum2
16	tpd	=	1.31226e-08	input = A3	output = sum3
17	tpd	=	1.47743e-08	input = B0	output = sum0
18	tpd	=	1.91460e-08	input = B0	output = sum1
19	tpd	=	1.96785e-08	input = B0	output = sum2
20	tpd	=	1.96914e-08	input = B0	output = sum3
21	tpd	=	1.47743e-08	input = B1	output = sum0
22	tpd	=	1.91460e-08	input = B1	output = sum1
23	tpd	=	1.96785e-08	input = B1	output = sum2
24	tpd	=	1.96914e-08	input = B1	output = sum3
25	tpd	=	1.47743e-08	input = B2	output = sum0
26	tpd	=	1.91460e-08	input = B2	output = sum1
27	tpd	=	1.96785e-08	input = B2	output = sum2
28	tpd	=	1.96914e-08	input = B2	output = sum3
29	tpd	=	1.47743e-08	input = B3	output = sum0
30	tpd	=	1.91460e-08	input = B3	output = sum1
31	tpd	=	1.96785e-08	input = B3	output = sum2
32	tpd	=	1.96914e-08	input = B3	output = sum3
33					


subtractor delays

Delay Analysis >  subtractor.txt				
1	tpd	=	5.71699e-09	input = A0 output = sum0
2	tpd	=	5.71699e-09	input = A0 output = sum1
3	tpd	=	5.71699e-09	input = A0 output = sum2
4	tpd	=	5.71699e-09	input = A0 output = sum3
5	tpd	=	5.71699e-09	input = A1 output = sum0
6	tpd	=	5.71699e-09	input = A1 output = sum1
7	tpd	=	5.71699e-09	input = A1 output = sum2
8	tpd	=	5.71699e-09	input = A1 output = sum3
9	tpd	=	5.71699e-09	input = A2 output = sum0
10	tpd	=	5.71699e-09	input = A2 output = sum1
11	tpd	=	5.71699e-09	input = A2 output = sum2
12	tpd	=	5.71699e-09	input = A2 output = sum3
13	tpd	=	5.71699e-09	input = A3 output = sum0
14	tpd	=	5.71699e-09	input = A3 output = sum1
15	tpd	=	5.71699e-09	input = A3 output = sum2
16	tpd	=	5.71699e-09	input = A3 output = sum3
17	tpd	=	5.71699e-09	input = B0 output = sum0
18	tpd	=	5.71699e-09	input = B0 output = sum1
19	tpd	=	5.71699e-09	input = B0 output = sum2
20	tpd	=	5.71699e-09	input = B0 output = sum3
21	tpd	=	5.71699e-09	input = B1 output = sum0
22	tpd	=	5.71699e-09	input = B1 output = sum1
23	tpd	=	5.71699e-09	input = B1 output = sum2
24	tpd	=	5.71699e-09	input = B1 output = sum3
25	tpd	=	5.71699e-09	input = B2 output = sum0
26	tpd	=	5.71699e-09	input = B2 output = sum1
27	tpd	=	5.71699e-09	input = B2 output = sum2
28	tpd	=	5.71699e-09	input = B2 output = sum3
29	tpd	=	5.71699e-09	input = B3 output = sum0
30	tpd	=	5.71699e-09	input = B3 output = sum1
31	tpd	=	5.71699e-09	input = B3 output = sum2
32	tpd	=	5.71699e-09	input = B3 output = sum3
33				


less than delays

Delay Analysis >  lesser_comparator.txt				
1	tpd	=	2.41307e-08	input = A0 output = AlessB
2	tpd	=	2.41307e-08	input = A1 output = AlessB
3	tpd	=	2.41307e-08	input = A2 output = AlessB
4	tpd	=	2.41307e-08	input = A3 output = AlessB
5	tpd	=	2.58454e-08	input = B0 output = AlessB
6	tpd	=	2.58454e-08	input = B1 output = AlessB
7	tpd	=	2.58454e-08	input = B2 output = AlessB
8	tpd	=	2.58454e-08	input = B3 output = AlessB


more than delays

Delay Analysis >  greater_comparator.txt					
1	tpd	=	2.39790e-08	input = A0	output = AmoreB
2	tpd	=	2.39790e-08	input = A1	output = AmoreB
3	tpd	=	2.39790e-08	input = A2	output = AmoreB
4	tpd	=	2.39790e-08	input = A3	output = AmoreB
5	tpd	=	2.32674e-08	input = B0	output = AmoreB
6	tpd	=	2.32674e-08	input = B1	output = AmoreB
7	tpd	=	2.32674e-08	input = B2	output = AmoreB
8	tpd	=	2.32674e-08	input = B3	output = AmoreB

equal to delays

Delay Analysis >  equals_comparator.txt					
1	tpd	=	2.90845e-08	input = A0	output = AequalsB
2	tpd	=	2.90845e-08	input = A1	output = AequalsB
3	tpd	=	2.90845e-08	input = A2	output = AequalsB
4	tpd	=	2.90845e-08	input = A3	output = AequalsB
5	tpd	=	2.50111e-08	input = B0	output = AequalsB
6	tpd	=	2.50111e-08	input = B1	output = AequalsB
7	tpd	=	2.50111e-08	input = B2	output = AequalsB
8	tpd	=	2.50111e-08	input = B3	output = AequalsB


and delays


Delay Analysis >  delay_and.txt				
1	tpd	=	5.93404e-09	input = A0 output = and_oper_out0
2	tpd	=	5.93496e-09	input = A0 output = and_oper_out1
3	tpd	=	5.92186e-09	input = A0 output = and_oper_out2
4	tpd	=	5.90653e-09	input = A0 output = and_oper_out3
5	tpd	=	5.93404e-09	input = A1 output = and_oper_out0
6	tpd	=	5.93496e-09	input = A1 output = and_oper_out1
7	tpd	=	5.92186e-09	input = A1 output = and_oper_out2
8	tpd	=	5.90653e-09	input = A1 output = and_oper_out3
9	tpd	=	5.93404e-09	input = A2 output = and_oper_out0
10	tpd	=	5.93496e-09	input = A2 output = and_oper_out1
11	tpd	=	5.92186e-09	input = A2 output = and_oper_out2
12	tpd	=	5.90653e-09	input = A2 output = and_oper_out3
13	tpd	=	5.93404e-09	input = A3 output = and_oper_out0
14	tpd	=	5.93496e-09	input = A3 output = and_oper_out1
15	tpd	=	5.92186e-09	input = A3 output = and_oper_out2
16	tpd	=	5.90653e-09	input = A3 output = and_oper_out3
17	tpd	=	5.72707e-09	input = B0 output = and_oper_out0
18	tpd	=	5.74510e-09	input = B0 output = and_oper_out1
19	tpd	=	5.72853e-09	input = B0 output = and_oper_out2
20	tpd	=	5.71699e-09	input = B0 output = and_oper_out3
21	tpd	=	5.72707e-09	input = B1 output = and_oper_out0
22	tpd	=	5.74510e-09	input = B1 output = and_oper_out1
23	tpd	=	5.72853e-09	input = B1 output = and_oper_out2
24	tpd	=	5.71699e-09	input = B1 output = and_oper_out3
25	tpd	=	5.72707e-09	input = B2 output = and_oper_out0
26	tpd	=	5.74510e-09	input = B2 output = and_oper_out1
27	tpd	=	5.72853e-09	input = B2 output = and_oper_out2
28	tpd	=	5.71699e-09	input = B2 output = and_oper_out3
29	tpd	=	5.72707e-09	input = B3 output = and_oper_out0
30	tpd	=	5.74510e-09	input = B3 output = and_oper_out1
31	tpd	=	5.72853e-09	input = B3 output = and_oper_out2
32	tpd	=	5.71699e-09	input = B3 output = and_oper_out3

magic :





Adder subtractor

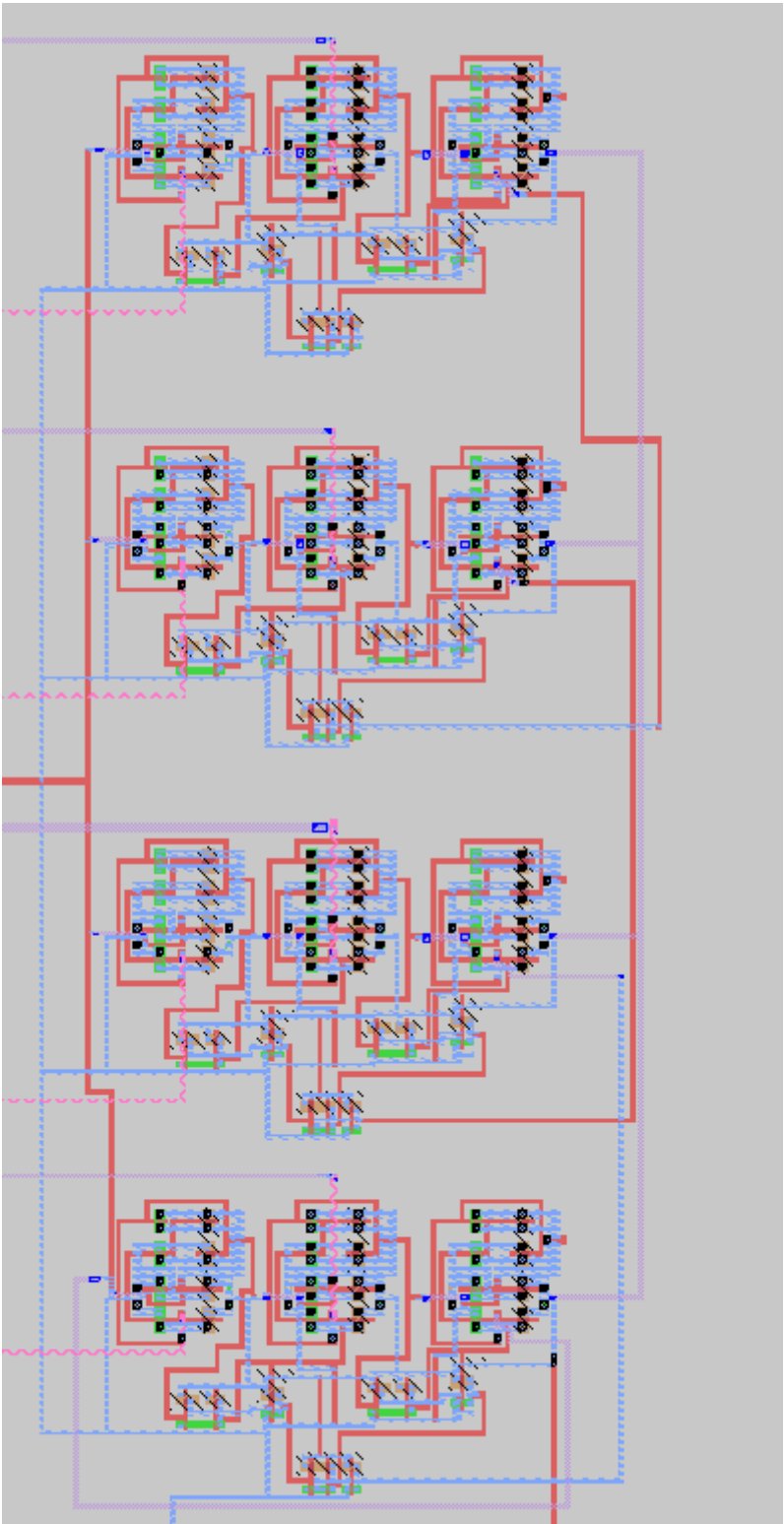

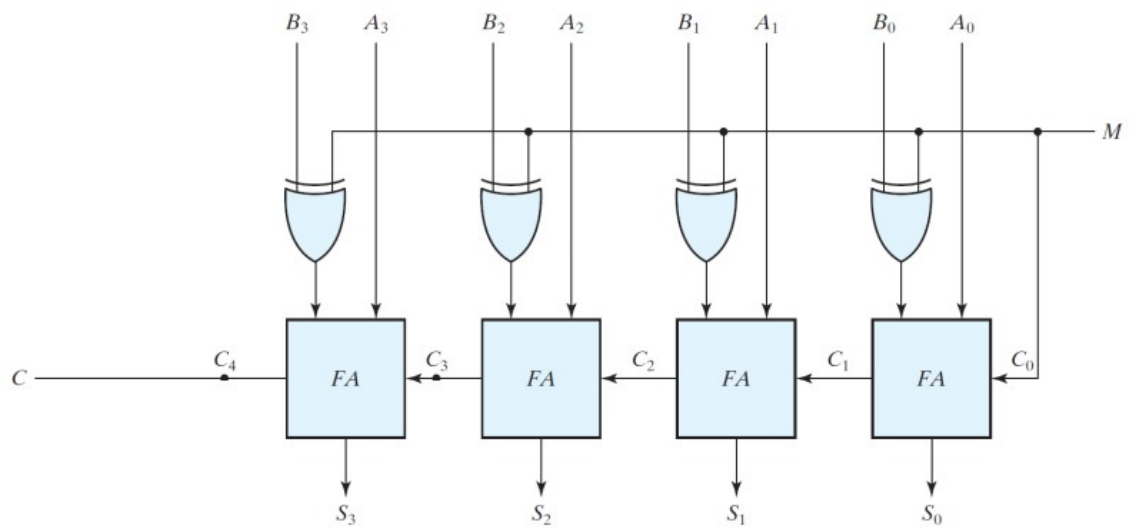



comparator

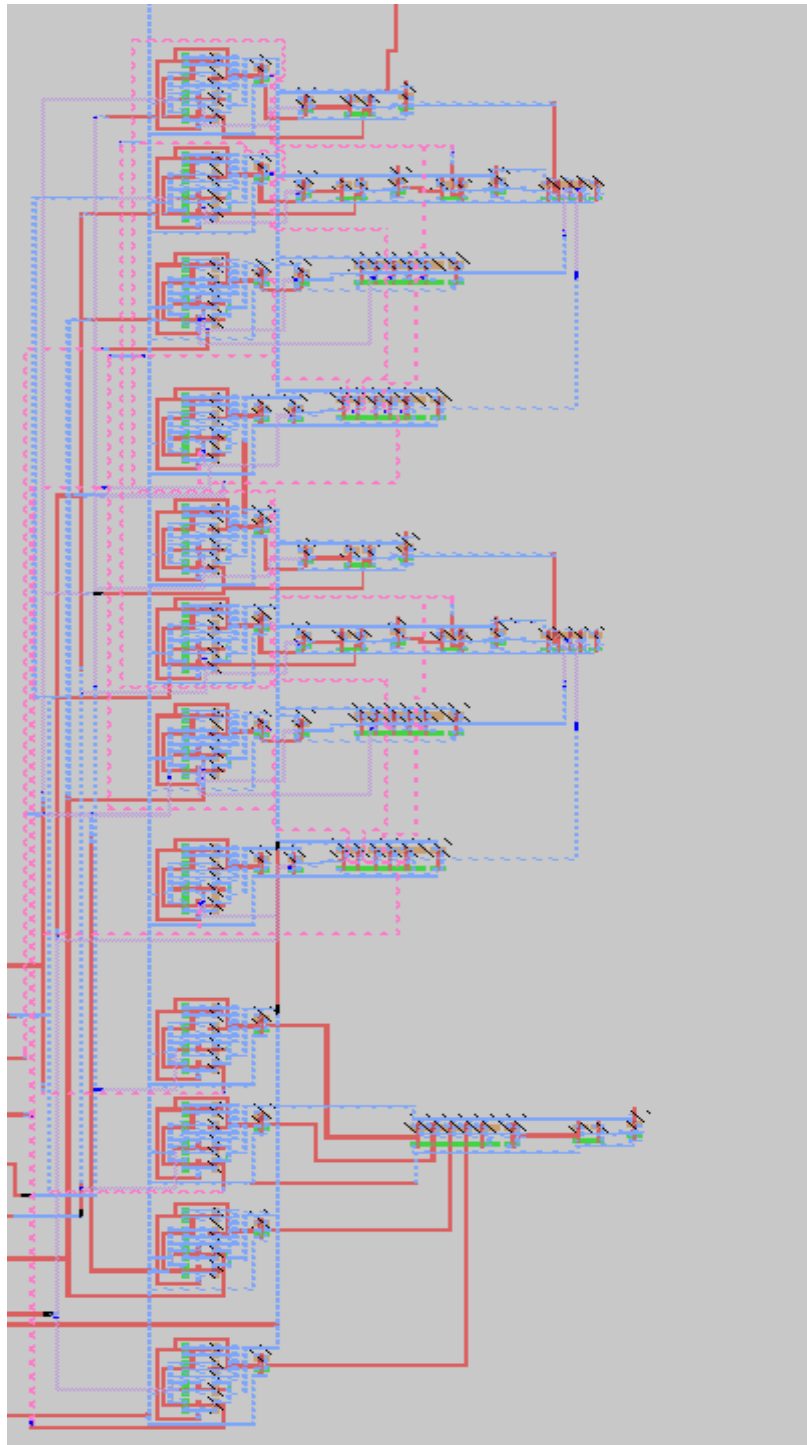

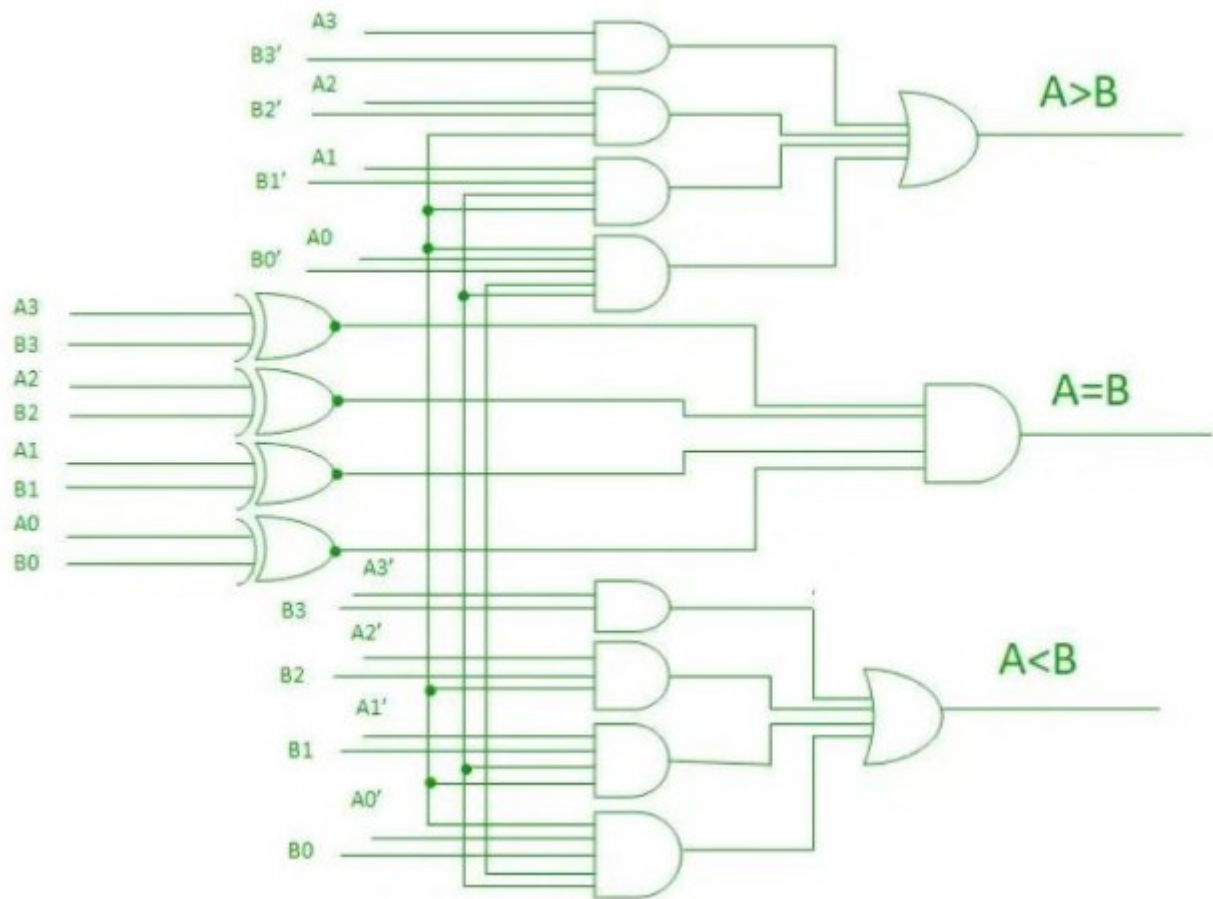



and block:

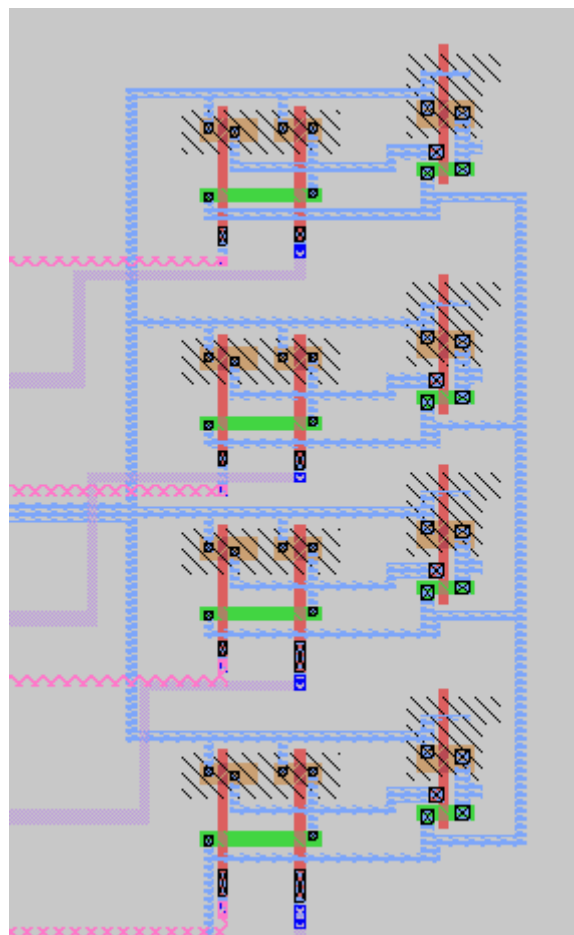

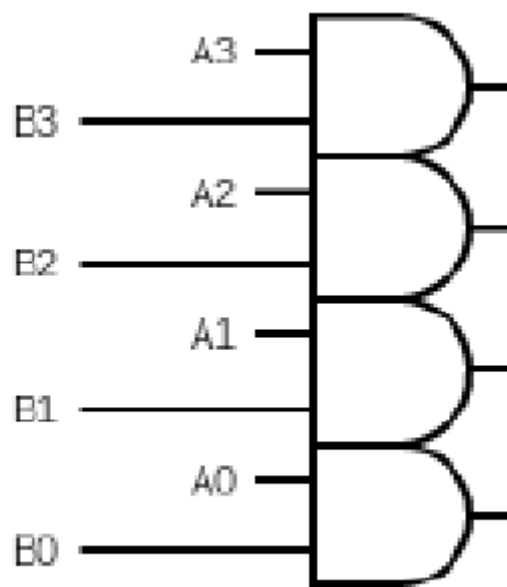



decoder:

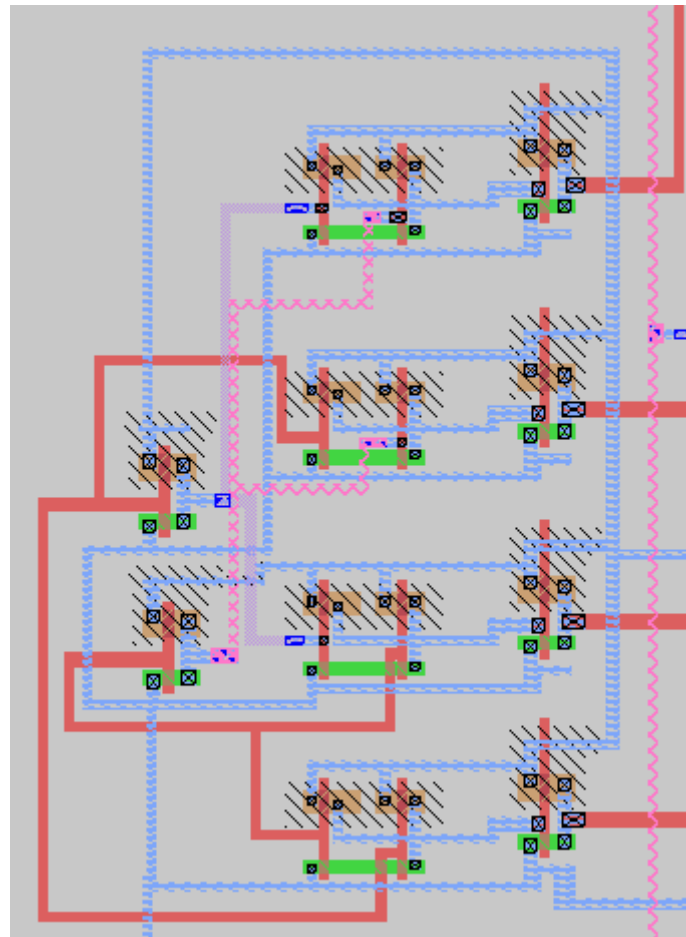

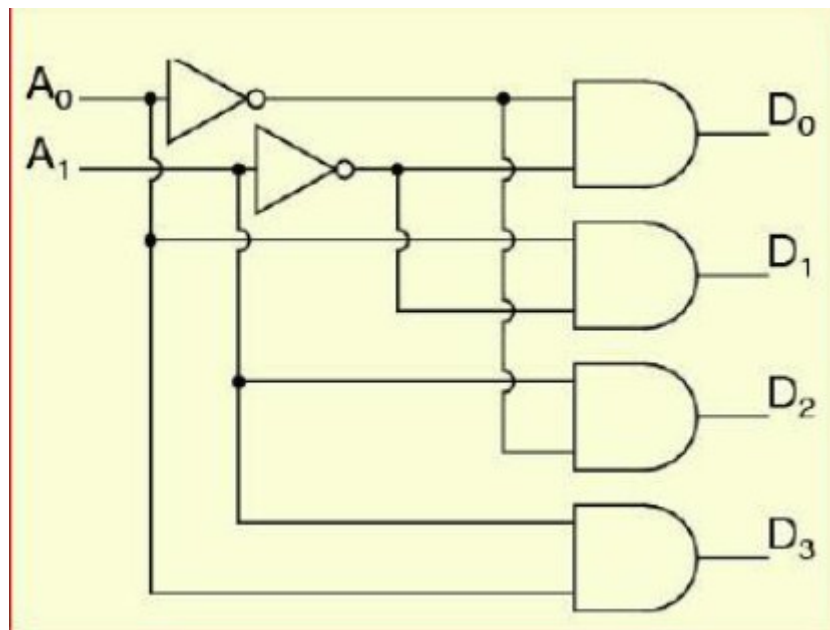

one of the enable:

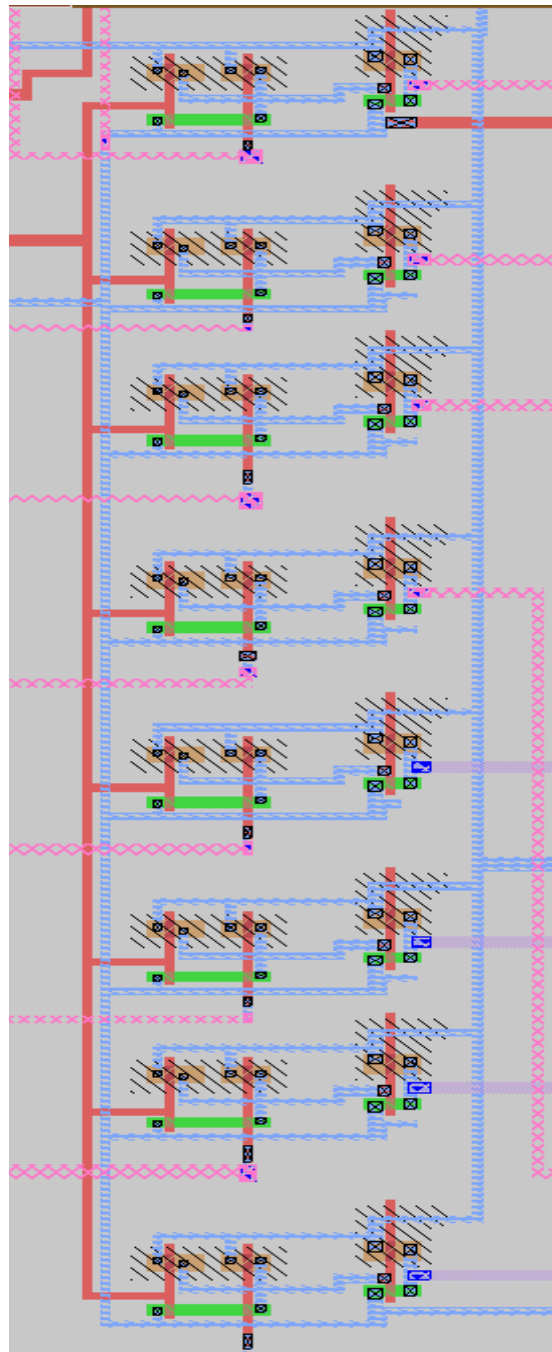

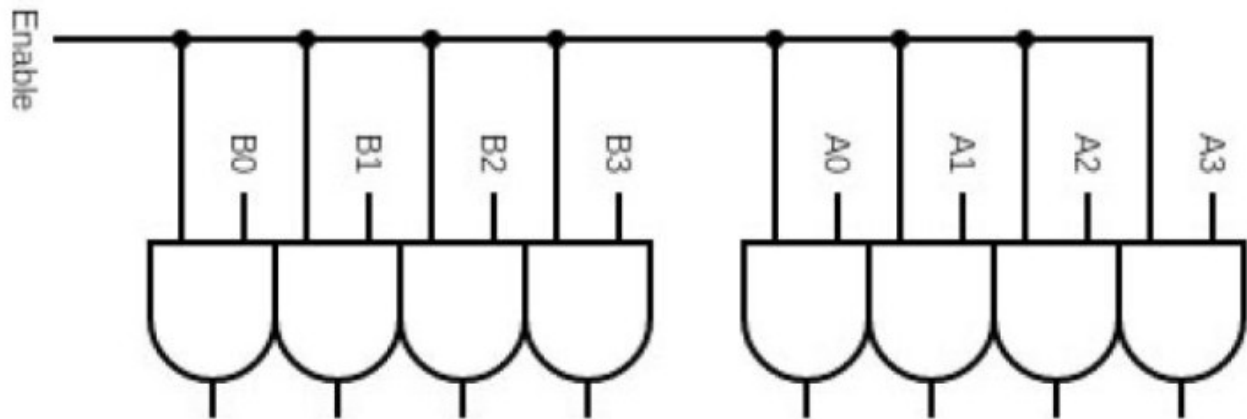

Issues with the magic:

label on my magic doesn't show up, I have to zoom in completely to see.  
 There's a lot of delays and overshoot in my adder subtractor magic

Enable of adder subtractor

-I took D0 and D1 from the decoder and OR'd it

-In my comparator :

even when enable is low for comparator, AequalsB will show high since my inputs then would be a- 0000 and b- 0000.

In order to avoid it, I AND'd the output with D3